 


## GATE Question Paper 2010, IN Question Number 42

### Question 42 Analysis

#### Question:

The logic gate circuit shown in the figure realizes the function



- (A) XOR    (B) XNOR    (C) Half adder    (D) Full adder

### Step-by-step Analysis of the Circuit

Let the inputs be:

- **X** and **Y** (two binary inputs)

Now examine the circuit:

- Top-left gate (AND):** Input:  $X, Y$   
Output =  $X \cdot Y$
- Bottom-left gate (NOR):** Input:  $X, Y$   
Output =  $\overline{X + Y}$
- Middle gate (NAND):** Input:  $X, Y$   
Output =  $\overline{X \cdot Y}$
- Final gate (OR):** Input: outputs from NOR and NAND gates  
Output =  $\overline{X + Y} + \overline{X \cdot Y}$

### Truth Table

X	Y	$\overline{X + Y}$	$\overline{X \cdot Y}$	$Z = \overline{X + Y} + \overline{X \cdot Y}$
0	0	1	1	1
0	1	0	1	1
1	0	0	1	1
1	1	0	0	0

This is the **truth table for XOR**.

## Final Answer

(A) XOR

## Brief Discussion

The circuit implements:

$$Z = \overline{X + Y} + \overline{X \cdot Y}$$

This matches the behavior of the XOR gate, which outputs 1 only when exactly one of the inputs is 1. Therefore, the circuit realizes the XOR logic function.